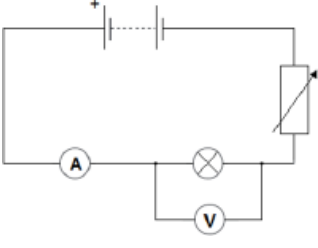


| Qu No. | | Extra Information | Marks |
|--------|--|--|----------------------------|
| 5.1 |  | <p>battery in series with bulb and ammeter</p> <p>voltmeter in parallel with the bulb</p> <p>variable resistor or variable power supply</p> | <p>1</p> <p>1</p> <p>1</p> |
| 5.2 | <p>correct pair of current readings at the same pd</p> <p>therefore</p> <p>current in lamp A is twice the current in lamp B</p> <p>so</p> <p>lamp A is twice as powerful and lamp B (hence is twice as bright)</p> | <p>eg at 10 V, $I_A = 0.74\text{A}$ and $I_B = 0.37\text{A}$</p> <p>must refer to power/rate of energy transfer</p> | <p>1</p> <p>1</p> <p>1</p> |
| 5.3 | <p>$R = V / I$</p> <p><u>Lowest</u></p> <p>$R = 0.6 / 0.1$</p> <p>$R = 6 \Omega$</p> <p><u>Highest</u></p> <p>$R = 10 / 0.74$</p> <p>$R = 13.5 \Omega$</p> <p>Difference = $13.5 - 6 = 7.5 \Omega$</p> | <p>allow $R = 1.0 / 0.16$</p> <p>$R = 6.25 \Omega$</p> <p>(other values may be acceptable but the values from the graph must be when $V \leq 1\text{V}$ and the lamp can reasonably be assumed to be ohmic)</p> <p>allow 7.25Ω if consistent</p> | <p>1</p> <p>1</p> <p>1</p> |